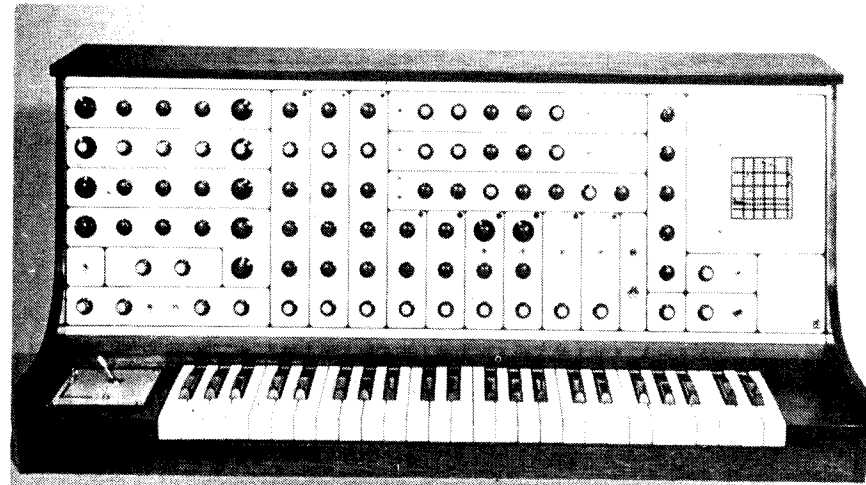


INTERNATIONAL MUSIC SYNTHESIZERS



ai 3600/4600

Constructional details of the mixer, noise generator/controller and main power supply are provided in this, the third article in the series.

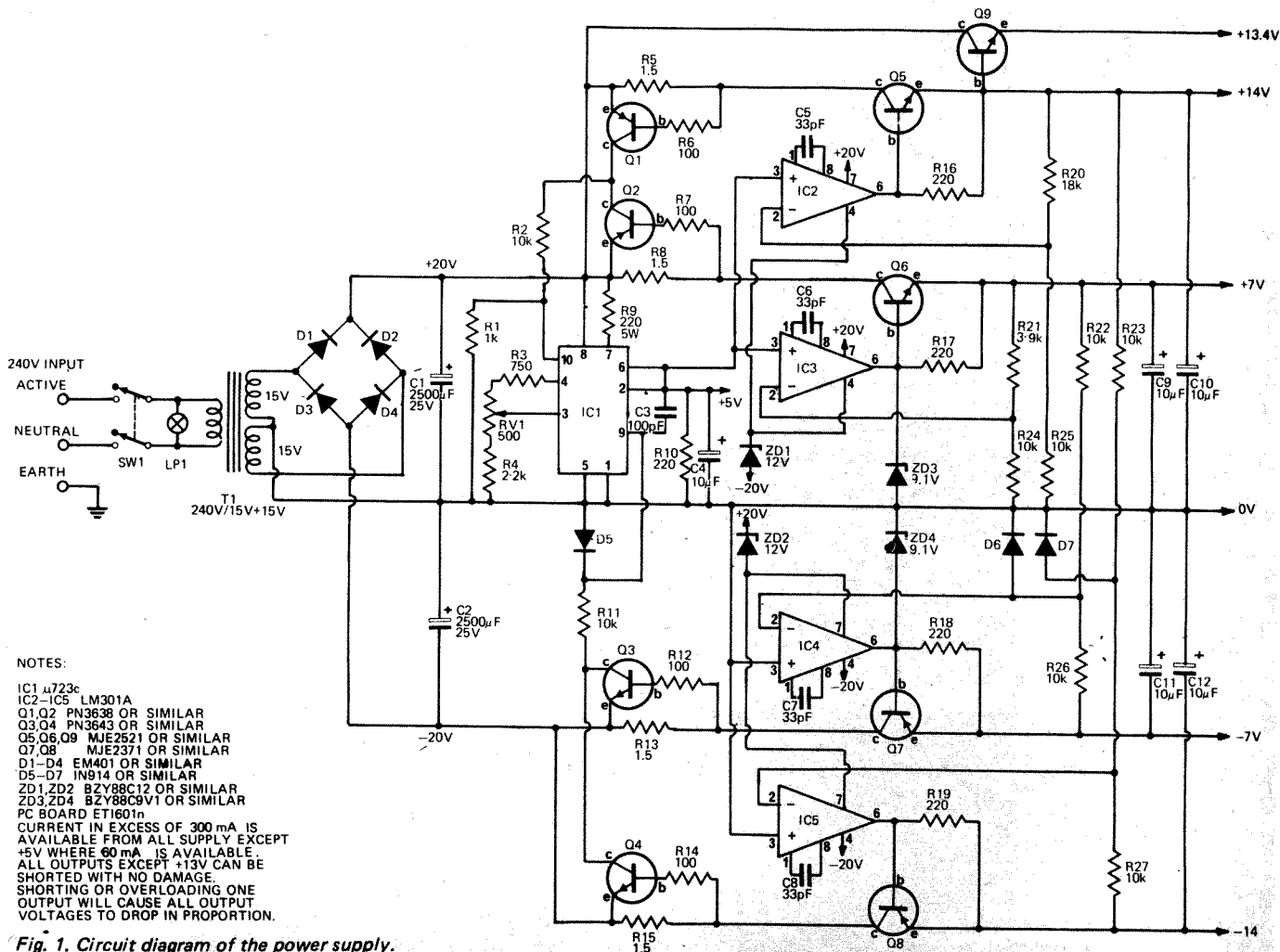


Fig. 1. Circuit diagram of the power supply.

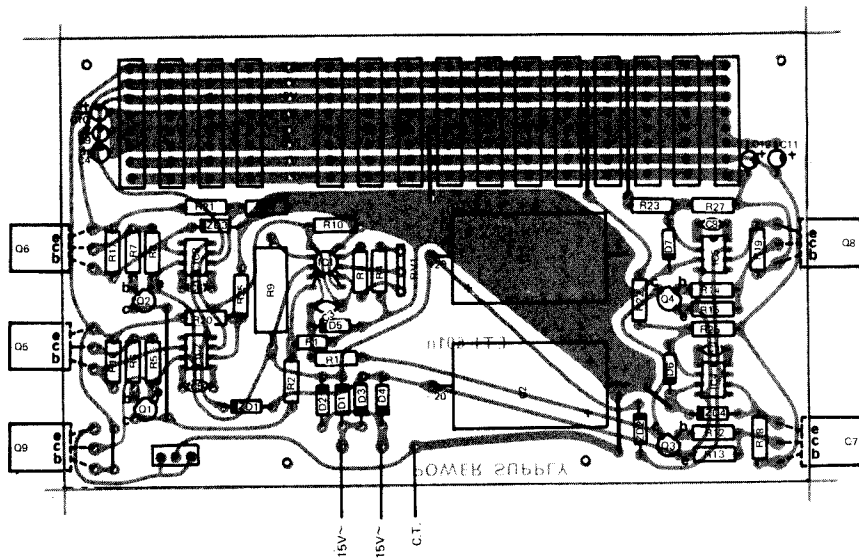


Fig. 2. Component overlay for power supply.

MODULES to be described this month are the mixer, noise generator and controller, and main power supply.

These three modules, together with those described last month enable the partly completed unit to be used to generate quite complex waveforms — and hence, sounds.


CONSTRUCTION Power Supply

Assemble the PC board with the aid of the component overlay Fig. 2. The power transistors should not be mounted at this time. Check the orientation of all the components especially checking the 723 regulator, the tag on the IC being next to pin 10.

The PC board is mounted by ¼ inch

spacers onto an aluminium panel Fig. 9 which is also the heatsink for the power transistors. The power transistor leads must be bent apart and up at right angles to pass through the PC board from the underside.

The heatsink should be used as a guide to determine the bending points. Since the transistors are on the underside of the PC board there must be no strain on the joints, otherwise the PC board track may be broken. Mount the transistors, using mica insulators, in position on the heatsink. The transistors may then be soldered to the PC board through the access holes provided. If required the heatsink may then be removed for other work to be carried out.

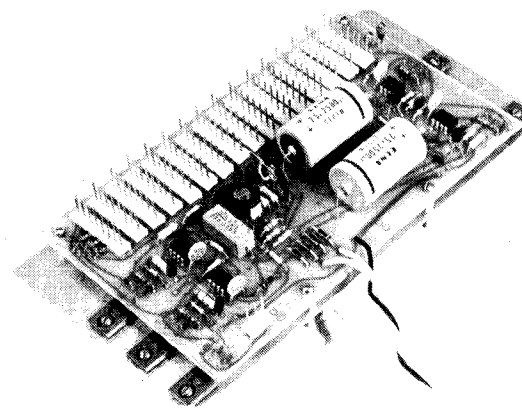

The method of construction of the power supply particularly mounting of the power transistors is shown in this photograph.


All assemblies and modules described in this, and last month's, article are used in the larger (4600) model synthesizer. Some of the components are used also in our smaller (3600) unit, but interconnections etc, are changed. Full details of this will be provided later.

Mixer

Assemble the PC board with the aid of the component overlay Fig. 4. Check the orientation of ICs and transistors. With the BC548-558 transistors there are two different pin connections used, depending on the manufacturer. National and Fairchild versions are the same and as shown on the overlay, whereas the Philips type is the reverse. The Philips type can be identified by the base (centre) lead, which is bent off centre, away from the flat. To use the National type bend the centre lead towards the flat.

The mechanical assembly is slightly different on this module than that for the oscillators. A metal plate is used to hold all the potentiometers (24) and three small brackets hold the PC board. The LED indicators are mounted on the front panel itself and are connected to the PC board either by soldering, or as recommended, by a plug and socket.


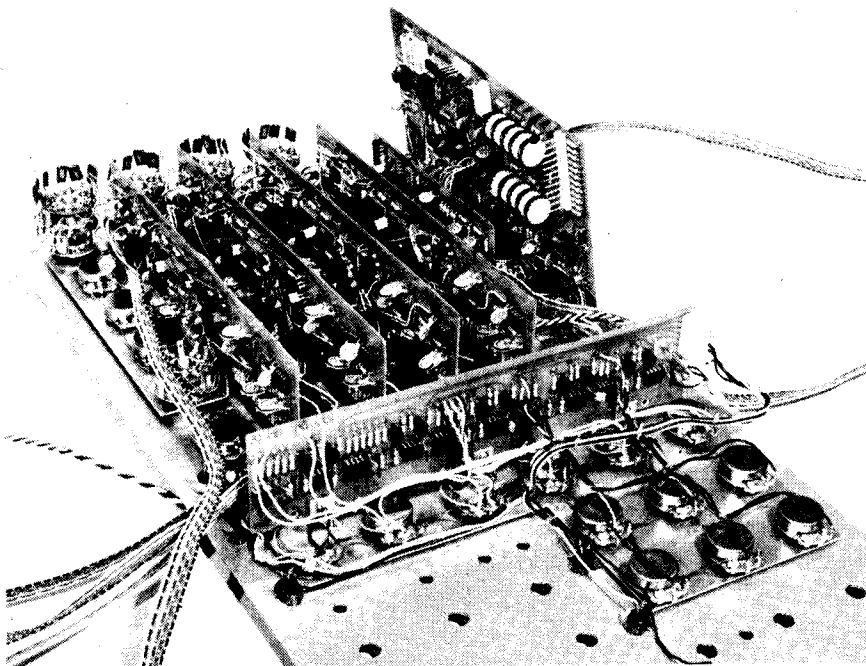
Each oscillator output is fed to three potentiometers on the mixer board. Five pads are provided on the PC board for connecting the common connection of each set of three potentiometers. A pin may also be fitted to each pad so that the oscillator connection may be disconnected if required.



The mixer and noise generator modules shown mounted in position.

INTERNATIONAL MUSIC SYNTHESIZERS

Fig. 3. Circuit diagram of a mixer stage.

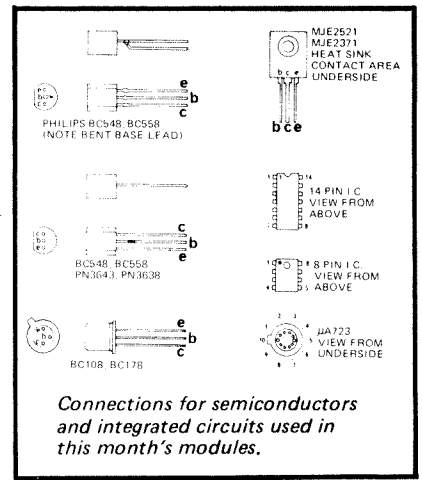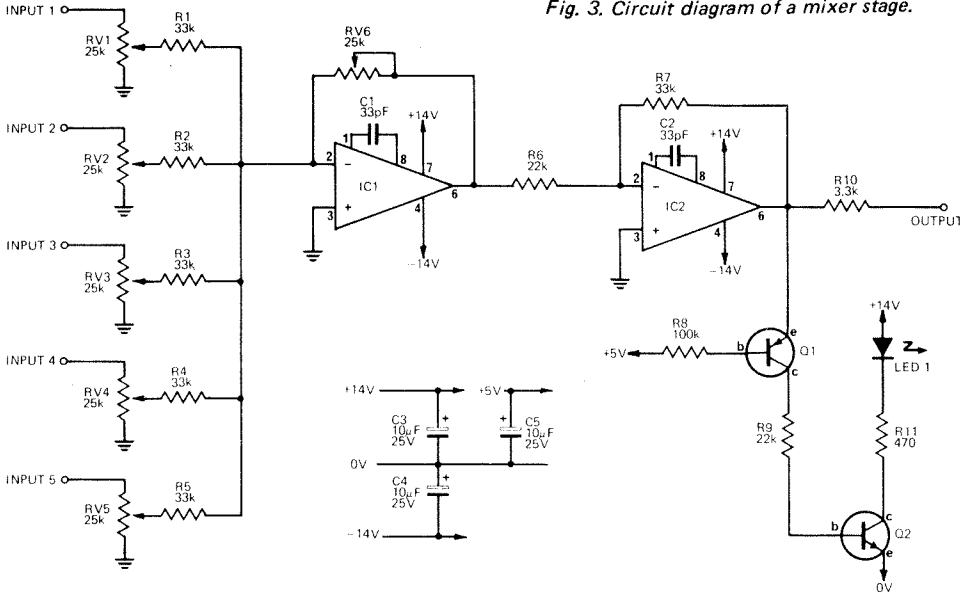

NOTES:

- MIXER 1 ONLY SHOWN, MIXERS 2-5 ARE SIMILAR EXCEPT MIXERS 4 AND 5 HAVE ONLY 2 INPUTS
- IC1 AND IC2 LM301A OR SIMILAR
- Q1 BC558 OR SIMILAR
- Q2 BC548 OR SIMILAR
- LEDs NSL 5023 OR SIMILAR
- COMPONENT NUMBERS FOR MIXERS 2-5 ARE AS FOLLOWS:
- MIXER 2: ADD 20 TO ALL NUMBERS I.E. R5 BECOMES R25
- MIXER 3: ADD 40 TO ALL NUMBERS I.E. R5 BECOMES R45
- MIXER 4: ADD 60 TO ALL NUMBERS I.E. R5 BECOMES R65
- MIXER 5: ADD 80 TO ALL NUMBERS I.E. R5 BECOMES R85

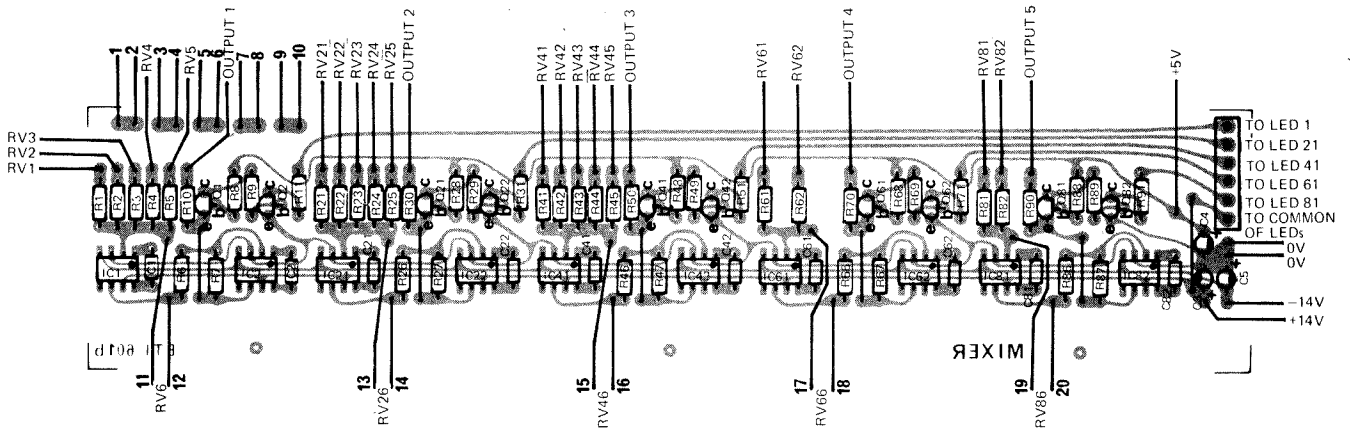


Fig. 4. Component overlay for mixer board.

Noise generator and controller


The construction of the module is very similar to that of the oscillator described last month.

Assemble the PC board with the aid of the component overlay, Fig. 7. It is recommended, that IC sockets are used for the CMOS. Make sure the integrated circuits and electrolytic capacitors are orientated correctly before soldering in place.

The PC board is then mounted on the metal bracket shown in Fig. 12. The bracket goes on the component side of the PC board to prevent any possibility of shorting the copper tracks. The two potentiometers and the switch may now be mounted and wired up. This bracket also holds the additional switch related to oscillator 4 which is wired up as shown in Fig. 8. The interconnection between this switch and that in oscillator 4 can be either by soldered leads or, a plug and socket can be used.

Soldering with power connected should be avoided along with accidental shorting of the outputs. The output can be shorted for a brief

Fig. 5. Wiring of potentiometers on mixer panel.

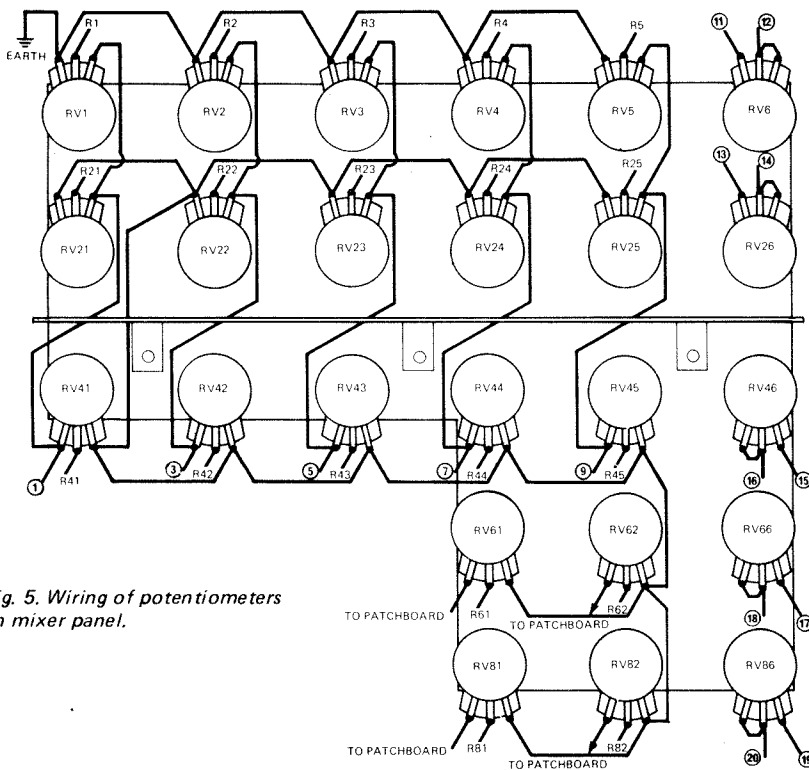

POWER SUPPLY – How it works

The power supply provides regulated outputs of +14V, +7V, +5V, -7V and -14V. The 5V supply can deliver 60 mA and all other outputs 300 mA. An additional output of +13.4V is provided to supply the high current requirement of the headphone output amplifier.

The rectifier and filter is a conventional system supplying $\pm 20V$. The 5V output is derived from a $\mu A723C$, voltage regulator (IC1) which has very good temperature and load regulation. The +5 volts is used as the main reference for the other supplies. Current limitation is provided for by R9 which limits the current to about 85 mA. The output is adjustable by RV1 such that exactly 5V can be obtained.

The output of IC1 can be shutdown in either of two modes. A positive current into pin 10 or a negative current out of pin 9 will cause the output voltage to drop to zero. Use of this is made in the overload network of the other supply outputs.

The +7V output is via a series pass transistor, Q6, which is controlled by IC3, a high gain differential amplifier which is used as a comparator. The non-inverting input (positive) of IC3 is connected to the +5V output where, in addition, the inverting (negative) input, is connected via a 5/7 divider R21/24. The result of this connection is that the output will stabilize at +7V. The high gain of IC3 will keep this voltage constant with nominal load and supply voltage changes.

A current sensing resistor, R8, is in series with the collector of Q6. If the voltage across this resistor exceeds 0.6V, the base emitter of Q2 will become forward biased, turning it on. This causes a positive current to flow into pin 10 of IC1 shutting it down. Since the output of the +7V regulator is referred to the +5V output, the +7V supply will also shut down and the output current will be limited to about 400 mA. To prevent over voltage from the +7V supply on

switch on, the output is limited by ZD3 to about 8.5 volts.

The -7V supply is similar to the +7V supply, except that the reference voltage is now zero volts, (pin 3) and this is compared to a voltage at the junction of R26 and R22. The voltage will be zero when the output of the -7V is identical to the +7V but of opposite polarity. Diode D6 is used to protect the input of IC4. Overload on this output turns on Q3 which removes current from pin 9 of IC1 shutting it down. This shuts down the +7V supply and since the -7V "tracks" the +7V output, it also will shut down.

The $\pm 14V$ supplies are identical to the $\pm 7V$ supplies except for the sensing resistors R20/25 on the +14V supply.

The +13.4V output is simply an emitter follower on the +14V rail. This supply should not however be shorted since no protection is provided.

MIXER – How it works

The mixer used is quite conventional, using an IC (IC1) to sum the input currents. Individual gain control is provided by RV1-5 and overall gain by RV6. Since the output of this type of mixer is inverted an additional IC is used to reinvert the signal.

Overload indication is provided by Q1, Q2 and LED1. If the output voltage exceeds 5.6V, Q1 becomes forward biased and Q1 and Q2 turn on, illuminating the LED indicator. The base resistor R8 prevents damage to Q1 should the output swing negative. The overload point as indicated by the LED is chosen to protect the inputs of following stages from being overloaded. The mixer itself has an overload point of about 12V.

Mixers 1,2, and 3 are identical whereas mixers 4 and 5, although otherwise identical, have only 2 inputs. The inputs of mixers 1,2, and 3 are wired directly to the outputs of the individual oscillators.

NOISE GENERATOR AND CONTROLLER – How it works

White noise is generated digitally by an 18 bit shift register which is clocked at about 35 kHz. Several feed-back loops around the shift register cause it to generate a pseudo-random bit pattern which closely approximates white noise.

The oscillator uses a quad, dual-input NOR CMOS gate (IC3), and although a NAND or inverter could be used in the circuit, it would not necessarily be a pin for pin replacement. Feedback is taken from the 5th, 9th and 18th stage in the shift register and these outputs are "mixed" by IC2 which is an exclusive OR gate, (see table) the output of which controls the 'D' input of the shift register. Resistor R1 and capacitor C1 are used to ensure that the system will start.

INPUTS		OUTPUTS
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

1 = HIGH LEVEL
0 = LOW LEVEL

The output of IC2/1, as well as being the control for the shift register, is the white noise we require. However, due to some unwanted components above 15 kHz, a low pass filter is used with a 15 kHz cutoff. To give an alternate "PINK" noise output, the filter is changed to cut frequencies above 500Hz with a 6 dB/octave slope. Since the output voltage will fall if some of the spectrum is removed, additional gain is also provided when 'PINK' noise is selected.

The controller is a completely separate function which is used to add a dc component to another signal or control voltage. This is done by mixing, in IC5, a percentage of the input signal and a percentage of a dc voltage. The output of IC5 is negative however, and must be inverted by IC6.

Fig. 6. Circuit diagram of Noise Generator and Controller.

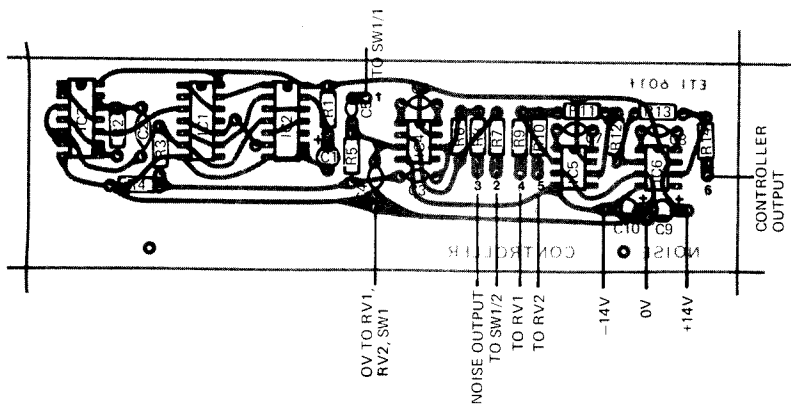
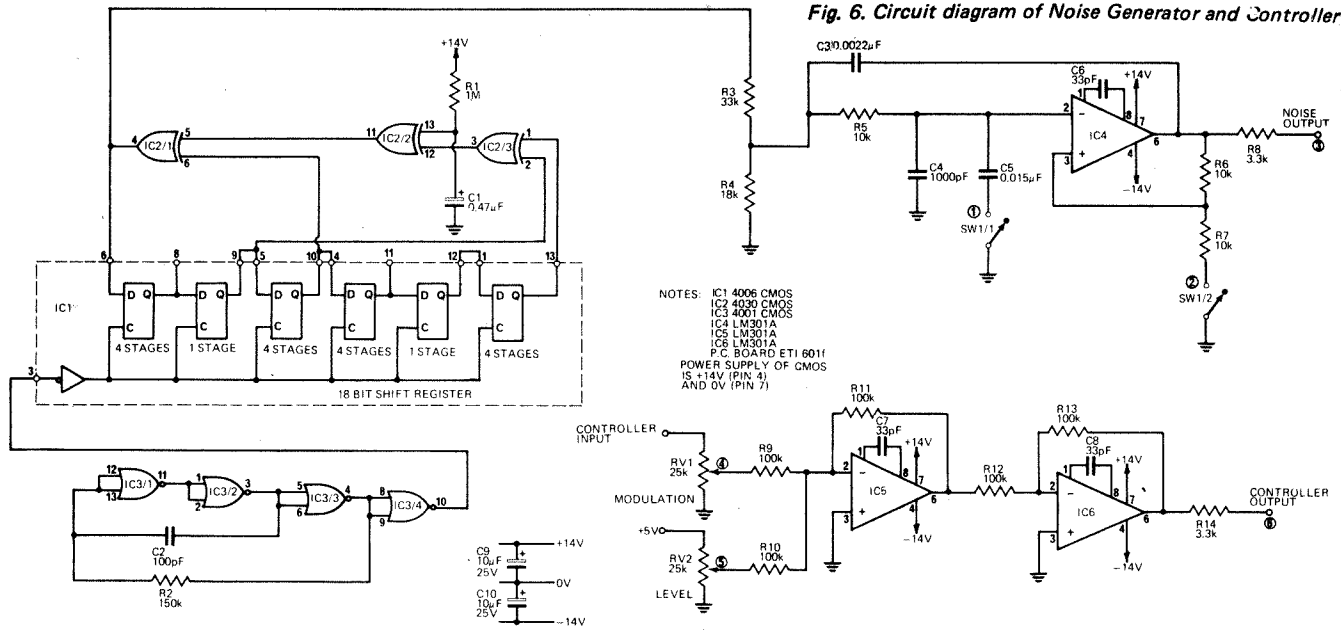


Fig. 7. Component overlay of Noise Generator and Controller.

INTERNATIONAL MUSIC SYNTHESIZERS


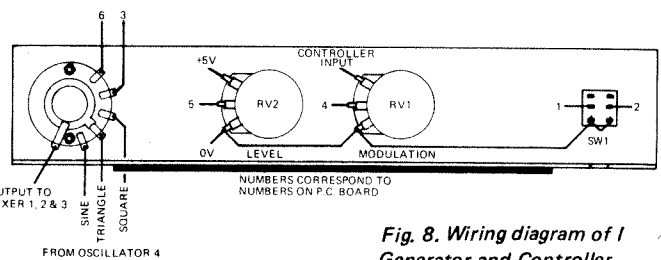


Fig. 8. Wiring diagram of I Generator and Controller.

Fig. 9. Heatsink for power supply.

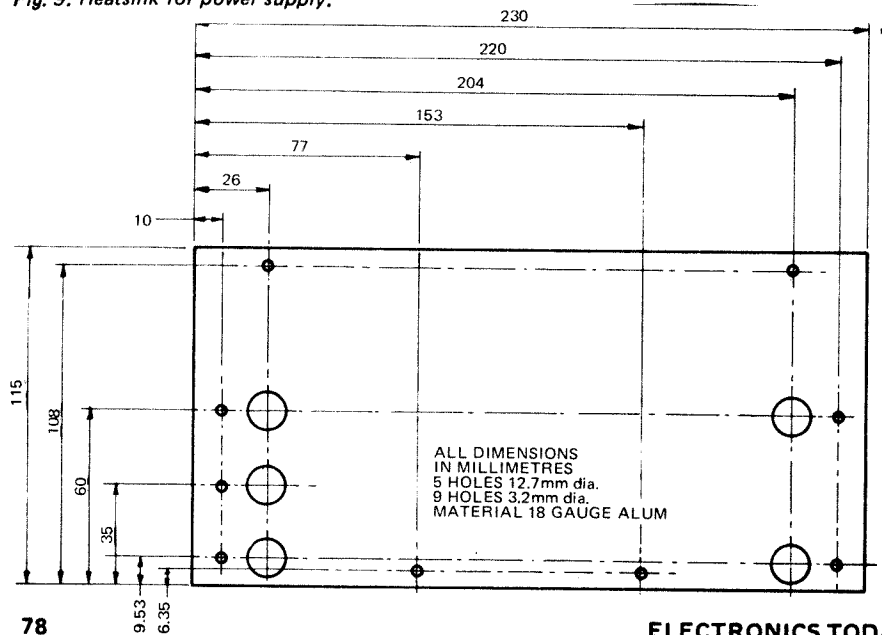

period without damage however this is not recommended.

The supply voltage to CMOS must never be reversed. This could cause the devices to destroy themselves.

Although the inputs of CMOS are internally protected against static charges, some care is still required in their handling. They should be stored in their aluminium carrier or in conductive plastic. They should be the last components added to the PC boards, preferably using IC sockets.

NEXT MONTH

Next month we will describe the Envelope Control, Transient 1 and Transient 2 modules. It is emphasised again that we are at present describing the larger synthesizer. The changes required for the smaller unit will be detailed later.

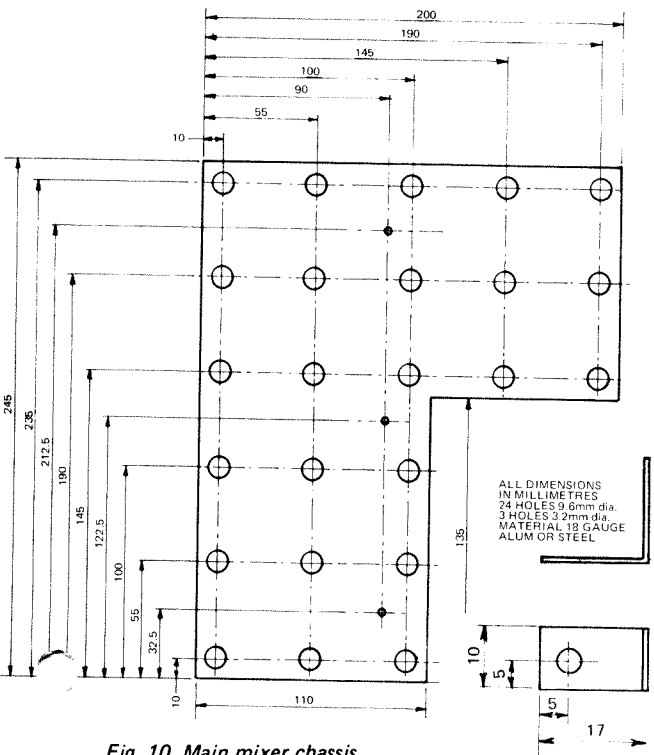


Fig. 10. Main mixer chassis.

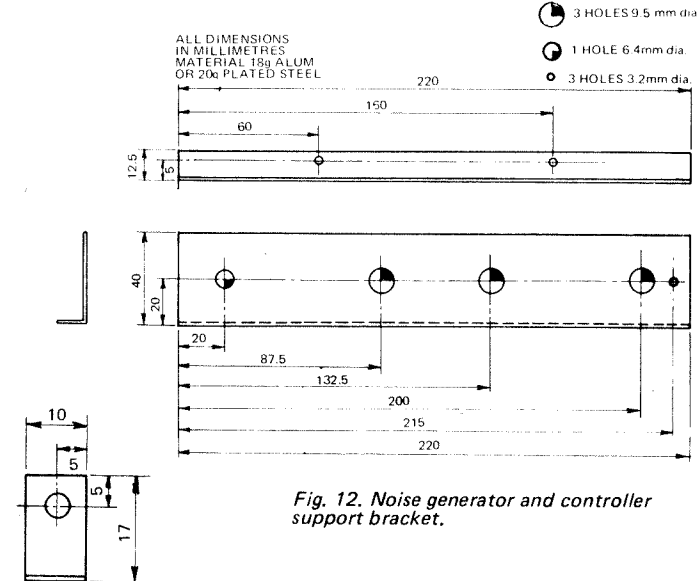


Fig. 11. Mixer board support bracket (three required).

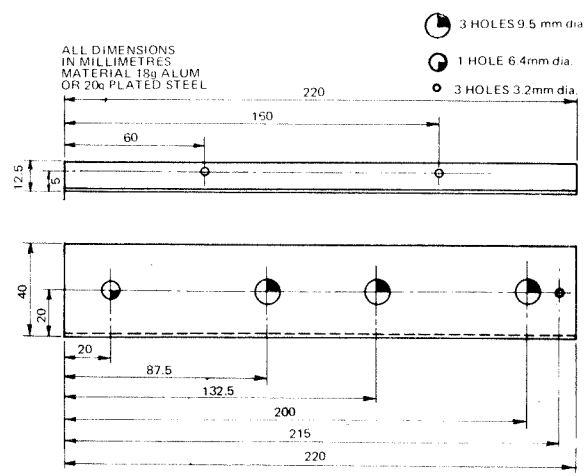


Fig. 12. Noise generator and controller support bracket.

PARTS LIST POWER SUPPLY

R1	Resistor	1k	1/4 W	5%
R2,11,22,23,24,25,26,27	"	10k	"	"
R3	"	750Ω	"	"
R4	"	2.2k	"	"
R5,8,13,15	"	1.5Ω	1/2 W	"
R6,7,12,14	"	100Ω	1/4 W	"
R9	"	220Ω	5 W	"
R10,16,17,18,19	"	220Ω	1/4 W	"
R20	"	18k	"	"
R21	"	3.9k	"	"
RV1	Potentiometer	500Ω	large trim type	
C1,2	Capacitor	2500μF	25 V electrolytic	
C3	"	100pF	ceramic	
C9,10	"	10μF	20V electrolytic	
C1,12	"		P.C. mounting	
C5,6,7,8	"	33pF	ceramic	
IC1	Integrated Circuit	μA723C	metal can type	
IC2,3,4,5	"	LM301A	minidip	
Q1,Q2	Transistor	PN3638	or similar	
Q3,4	"	PN3643	"	
Q5,6,9	"	MJE2521	"	
Q7,8	"	MJE2371	"	
D1-D4	Diode	EM401	or similar	
D5,6,7	"	IN914	"	
ZD1,2	Zener Diode	BZY88C12	"	
ZD3,4	"	BZY88C9V1	"	
T1	Transformer	240V primary	15 V-0-15 V sec @ .75A or more.	
SW1	Toggle Switch	DPDT	240 V rated	
LP1	240V Neon Indicator			
PC board	ET1 601 n			
Heatsink	as per Fig. 9.			
T05	heatsink for IC1			
4	1/4" spacers			
Recommended extras				
16	8 pin Utilux plugs	type A2402-8		
1	3 pin Utilux plug	type A2402-3		

PARTS LIST MIXER

R1,2,3,4,5,7	Resistor	33k	1/4 W	5%
R21,22,23,24,25,27	"	33k	"	"
R41,42,43,44,45,47	"	33k	"	"
R61,62,67	"	33k	"	"
R81,82,87	"	33k	"	"
R6,9,26,29,46	"	22k	"	"
R49,66,69,86,89	"	22k	"	"
R8,28,48,68,88	"	100k	"	"
R10,30,50,70,90	"	3.3k	"	"
R11,31,51,71,91	"	470	"	"
RV1-6	Potentiometer	25k	lin rotary	
RV21-26	"	25k	"	
RV41-46	"	25k	"	
RV61,62,66	"	25k	"	
RV81,82,86	"	25k	"	
C1,2,21,22,41	Capacitor	33pF	ceramic	
C42,61,62,81,82	"	33pF	"	
C3,4,5	"	10μF	20 V elect. PC mounting	
IC1, 2,21,22,41	Integrated Circuit	LM301A	minidip	
IC42,61,62,81,82	"	"	"	
Q1,21,41,61,81	Transistor	BC548, BC108	or similar	
Q2,22,42,62,82	"	BC558, BC178	or similar	
LED 1,21,41,61,81	light emitting diode	NSL5023	or similar	
PC board	ET1 601 b			
Metal chassis	as per Fig. 10			
3	brackets as per Fig. 11			
Recommended extras				
1	6 pin plug	Utilux type A2402-6		
1	6 pin socket	Utilux type M2139-6		
1	8 pin socket	Utilux type M2139-8		
14	pins	Utilux type M2138		

PARTS LIST NOISE CONTROLLER

R1	Resistor	1M	1/4 W	5%
R2	"	150k	"	"
R3	"	33k	"	"
R4	"	18k	"	"
R5,6,7	"	10k	"	"
R8,14	"	3.3k	"	"
R9,10,11,12,13	"	100k	"	"
RV1,2	Potentiometer	25k	lin rotary	
C1	Capacitor	0.47μF	25V elect. PC mounting	
C2	"	100pF	ceramic	
C3	"	0.0022	polyester	
C4	"	0.001	"	
C5	"	0.015	"	
C6,7,8	"	33pF	ceramic	
C9,10	"	10μF	20V elect. PC mounting	
IC1	Integrated Circuit	SCL4006AE*	CMOS	
IC2	"	SCL4030AE*	CMOS	
IC3	"	SCL4001AE*	CMOS	
IC4,5,6,	"	LM301A	minidip	
*The prefix and suffix of CMOS varies from manufacturer to manufacturer.				
SW1	Toggle switch	DPDT	C & K 7201	or similar
PC board ET1 601 f				
Metal bracket as per Fig. 12.				
Recommended extras				
3	14 pin IC sockets	Utilux type M1938-4	or similar	
1	8 pin molex socket	Utilux type M2139-8		
8	pins for above socket	Utilux type M2138		